

# Computation Structures - Lecture 7

Performance Measures



PersonalCompute.Net



## About

This document is part of the "**Computation Structures**" course, available at <https://PersonalCompute.net/resources/computation-structures>.

The objective of this course is to provide a solid foundation on the inner workings of computers, and how to use them efficiently. Practically, it tries to answer the question "*Why is my computer working like this?*" (where "like this" can mean "slow", "fast", "efficient" or "intermittently freezing").

Its intended audience is first and second-year university students, so its prerequisites are high-school levels of understanding for math and physics, and a beginner-level understanding of programming. It is also very useful to anyone whose job involves programming, but hasn't taken a formal course in Computer Architectures - a topic that is often overlooked in software or math-oriented degrees.

The **Course Contents** chapters use the materials from the original course (the MIT OpenCourseWare release), with very small changes (mostly cosmetic in nature).

Where existing, the **Real World Implications** chapters provide some additional context and explanations, not present in the MIT OpenCourseWare edition.

If you wish to download the "source code" for the course, go to <https://github.com/PersonalCompute-net/computation-structures/>.

## Credits

**Computation Structures (6.004), Spring 2017** - Original course content, from MIT OpenCourseWare.

Course led by Chris Terman, at MIT.

Originally published at <https://ocw.mit.edu/6-004S17> and <https://github.com/computation-structures/course/>.

Licensed under Creative Commons BY-NC-SA 4.0 - <https://ocw.mit.edu/terms>.

**Eisvogel** - LaTeX template and cover artwork.

Created by Pascal Wagler - <https://github.com/Wandmalfarbe/>.

Originally published at <https://github.com/Wandmalfarbe/pandoc-latex-template/>.

Licensed under BSD 3-clause license.

## Licensing

This work is licensed under a [Creative Commons](https://creativecommons.org/licenses/by-nc-sa/4.0/) "Attribution-NonCommercial-ShareAlike 4.0 International" license.




URL: <https://creativecommons.org/licenses/by-nc-sa/4.0/deed.en>

## Course Contents

In this lecture our goal is to introduce some metrics for measuring the performance of a circuit and then investigate ways to improve that performance. We'll start by putting aside circuits for a moment and look at an everyday example that will help us understand the proposed performance metrics.

### Forget Circuits... Let's Solve a Real Problem

#### Forget circuits... Let's Solve a Real Problem

 


**Figure 1.**

Laundry is a processing task we all have to face at some point! The input to our laundry “system” is some number of loads of dirty laundry and the output is the same loads, but washed, dried, and folded. There are two system components: a washer that washes a load of laundry in 30 minutes, and a dryer that dries a load in 60 minutes. You may be used to laundry system components with different propagation delays, but let's go with these delays for our example.

Our laundry follows a simple path through the system: each load is first washed in the washer and afterwards moved to the dryer for drying. There can, of course, be delays between the steps of loading the washer, or moving wet, washed loads to the dryer, or in taking dried loads out of the dryer. Let's assume we move the laundry through the system as fast as possible, moving loads to the next processing step as soon as we can.

## One Load at a Time

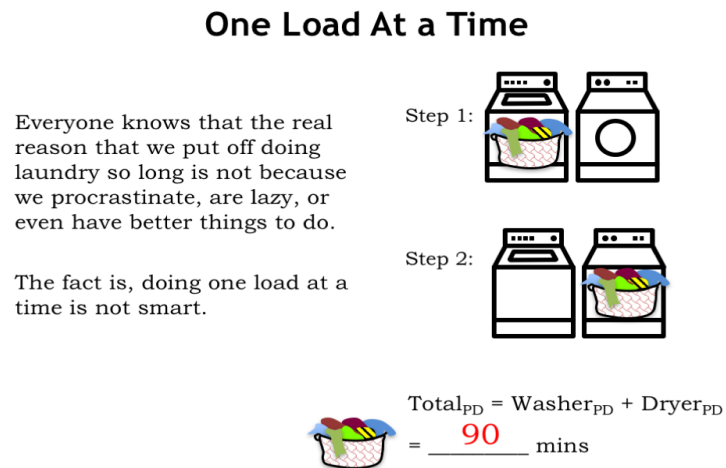


**Figure 2.**

Most of us wait to do laundry until we've accumulated several loads. That turns out to be a good strategy! Let's see why...

To process a single load of laundry, we first run it through the washer, which takes 30 minutes. Then we run it through the dryer, which takes 60 minutes. So the total amount of time from system input to system output is 90 minutes. If this were a combinational logic circuit, we'd say the circuit's propagation delay is 90 minutes from valid inputs to valid outputs.

Okay, that's the performance analysis for a single load of laundry. Now let's think about doing N loads of laundry.

## Doing N Loads of Laundry

 

**Figure 3.**


Here at MIT we like to make gentle fun of our colleagues at the prestigious institution just up the river from us. So here's how we imagine they do  $N$  loads of laundry at Harvard. They follow the combinational recipe of supplying new system inputs after the system generates the correct output from the previous set of inputs. So in step 1 the first load is washed and in step 2, the first load is dried, taking a total of 90 minutes. Once those steps complete, Harvard students move on to step 3, starting the processing of the second load of laundry. And so on...

The total time for the system to process  $N$  laundry loads is just  $N$  times the time it takes to process a single load. So the total time is  $N * 90$  minutes.

Of course, we're being silly here! Harvard students don't actually do laundry. Mummy sends the family butler over on Wednesday mornings to collect the dirty loads and return them starched and pressed in time for afternoon tea.

But I hope you're seeing the analogy we're making between the Harvard approach to laundry and combinational circuits. We can all see that the washer is sitting idle while the dryer is running and that inefficiency has a cost in terms of the rate at which  $N$  loads of laundry can move through the system.

## Doing N Loads... The 6.004 Way

 

**Figure 4.**

As engineering students here in 6.004, we see that it makes sense to overlap washing and drying. So in step 1 we wash the first load. And in step 2, we dry the first load as before, but, in addition, we start washing the second load of laundry. We have to allocate 60 minutes for step 2 in order to give the dryer time to finish. There’s a slight inefficiency in that the washer finishes its work early, but with only one dryer, it’s the dryer that determines how quickly laundry moves through the system.

Systems that overlap the processing of a sequence of inputs are called pipelined systems and each of the processing steps is called a stage of the pipeline. The rate at which inputs move through the pipeline is determined by the slowest pipeline stage. Our laundry system is a 2-stage pipeline with a 60-minute processing time for each stage.

We repeat the overlapped wash/dry step until all N loads of laundry have been processed. We’re starting a new washer load every 60 minutes and getting a new load of dried laundry from the dryer every 60 minutes. In other words, the effective processing rate of our overlapped laundry system is one load every 60 minutes. So once the process is underway N loads of laundry takes  $N*60$  minutes. And a particular load of laundry, which requires two stages of processing time, takes 120 minutes.

The timing for the first load of laundry is a little different since the timing of Step 1 can be shorter with no dryer to wait for. But in the performance analysis of pipelined systems, we’re interested in the steady state where we’re assuming that we have an infinite supply of inputs.

## Performance Measures

### Performance Measures

#### Latency:

The delay from when an input is established until the output associated with that input becomes valid.

$$\begin{array}{lcl} \text{Harvard Laundry} & = & \frac{90}{120} \text{ mins} \\ \text{6.004 Laundry} & = & \frac{120}{120} \text{ mins} \end{array} \quad \leftarrow \begin{array}{l} \text{Assuming that the} \\ \text{wash is started as} \\ \text{soon as possible and} \\ \text{waits (wet) in the} \\ \text{washer until dryer is} \\ \text{available.} \end{array}$$

#### Throughput:

The *rate* at which inputs or outputs are processed.

$$\begin{array}{lcl} \text{Harvard Laundry} & = & \frac{1/90}{1/60} \text{ outputs/min} \\ \text{6.004 Laundry} & = & \frac{1/60}{1/60} \text{ outputs/min} \end{array}$$

**Figure 5.**


We see that there are two interesting performance metrics. The first is the latency of the system, the time it takes for the system to process a particular input. In the Harvard laundry system, it takes 90 minutes to wash and dry a load. In the 6.004 laundry, it takes 120 minutes to wash and dry a load, assuming that it's not the first load.

The second performance measure is throughput, the rate at which the system produces outputs. In many systems, we get one set of outputs for each set of inputs, and in such systems, the throughput also tells us the rate at which inputs are consumed. In the Harvard laundry system, the throughput is 1 load of laundry every 90 minutes. In the 6.004 laundry, the throughput is 1 load of laundry every 60 minutes.

The Harvard laundry has lower latency, the 6.004 laundry has better throughput. Which is the better system? That depends on your goals! If you need to wash 100 loads of laundry, you'd prefer to use the system with higher throughput. If, on the other hand, you want clean underwear for your date in 90 minutes, you're much more concerned about the latency.

The laundry example also illustrates a common tradeoff between latency and throughput. If we increase throughput by using pipelined processing, the latency usually increases since all pipeline stages must operate in lock-step and the rate of processing is thus determined by the slowest stage.

## Okay, Back to Circuits...

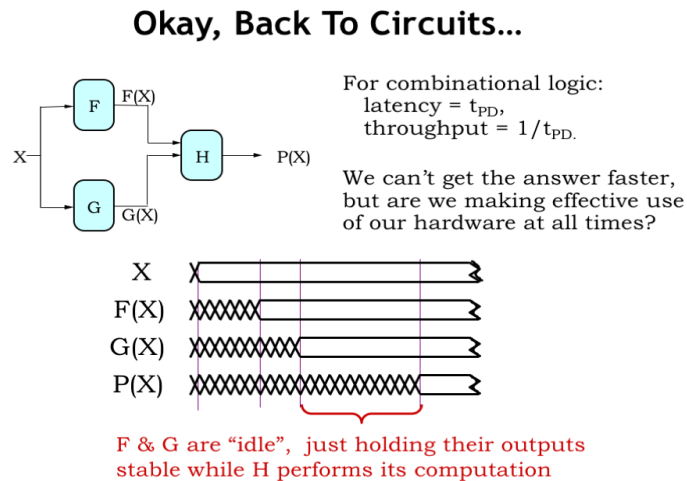

**Figure 6.**


Okay, now let's apply all this analysis to improving the performance of our circuits. The latency of a combinational logic circuit is simply its propagation delay  $t_{PD}$ . And the throughput is just  $1/t_{PD}$  since we start processing the next input only after finishing the computation on the current input.

Consider a combinational system with three components: F, G, and H, where F and G work in parallel to produce the inputs to H. Using this timing diagram we can follow the processing of a particular input value X. Sometime after X is valid and stable, the F and G modules produce their outputs F(X) and G(X).

Now that the inputs to H are valid and stable, the H module will produce the system output  $P(X)$  after a delay set by the propagation delay of H. The total elapsed time from valid input to valid output is determined by the propagation delays of the component modules. Assuming we use those modules as-is, we can't make any improvements on this latency.

But what about the system's throughput? Observe that after producing their outputs, the F and G modules are sitting idle, just holding their outputs stable while H performs its computation. Can we figure out a way for F and G to get started processing the next input while still letting H do its job on the first input? In other words, can we divide the processing of the combinational circuit into two stages where the first stage computes  $F(X)$  and  $G(X)$ , and the second stage computes  $H(X)$ ? If we can, then we can increase the throughput of the system.

## Pipelined Cicuits

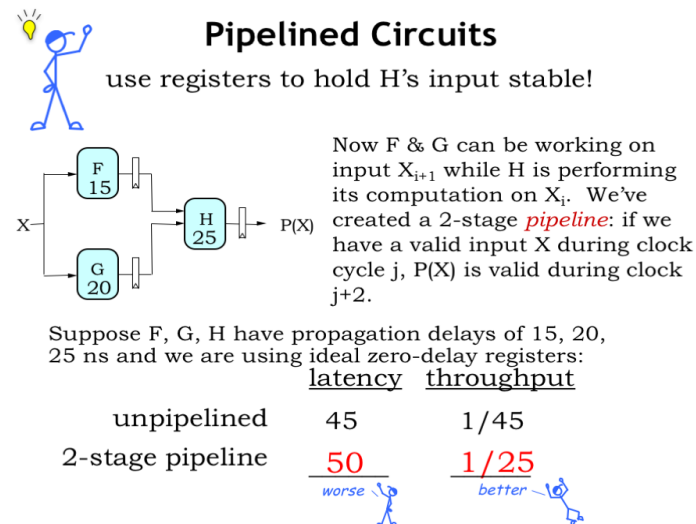

**Figure 7.**


Mr. Blue's inspiration is to use registers to hold the values  $F(X)$  and  $G(X)$  for use by H, while the F and G modules start working on the next input value. To make our timing analysis a little easier, we'll assume that our pipelining registers have a zero propagation delay and setup time.

The appropriate clock period for this sequential circuit is determined by the propagation delay of the slowest processing stage. In this example, the stage with F and G needs a clock period of at least 20 ns to work correctly. And the stage with H needs a clock period of 25 ns to work correctly. So the second stage is the slowest and sets the system clock period at 25 ns.

This will be our general plan for increasing the throughput of combinational logic: we'll use registers to divide the processing into a sequence of stages, where the registers capture the outputs from one processing stage and hold them as inputs for the next processing stage. A particular input will progress through the system at the rate of one stage per clock cycle.

In this example, there are two stages in the processing pipeline and the clock period is 25 ns, so the latency of the pipelined system is 50 ns, i.e., the number of stages times the system's clock period. The latency of the pipeline system is a little longer than the latency of the unpipelined system. However, the pipeline system produces 1 output every clock period, or 25 ns. The pipeline system has considerably better throughput at the cost of a small increase in latency.

## Pipeline Diagrams

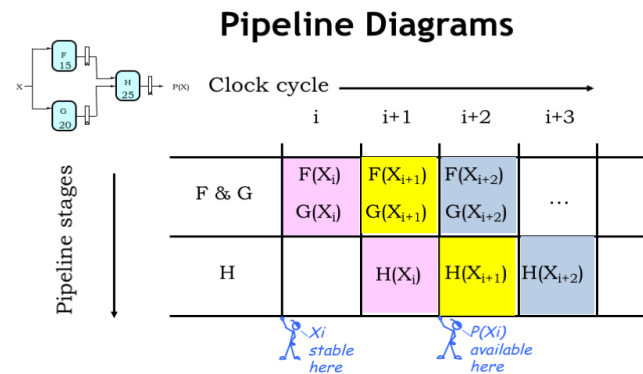

The results associated with a particular set of input data moves *diagonally* through the diagram, progressing through one pipeline stage each clock cycle.

**Figure 8.**

Pipeline diagrams help us visualize the operation of a pipelined system. The rows of the pipeline diagram represent the pipeline stages and the columns are successive clock cycles.

At the beginning of clock cycle  $i$  the input  $X_i$  becomes stable and valid. Then during clock cycle  $i$  the F and G modules process that input and at the end of the cycle the results  $F(X_i)$  and  $G(X_i)$  are captured by the pipeline registers between the first and second stages.

Then in cycle  $i + 1$ , H uses the captured values to do its share of the processing of  $X_i$ . And, meanwhile, the F and G modules are working on  $X_{i+1}$ . You can see that the processing for a particular input value moves diagonally through the diagram, one pipeline stage per clock cycle.

At the end of cycle  $i + 1$ , the output of H is captured by the final pipeline register and is available for use during cycle  $i + 2$ . The total time elapsed between the arrival of an input and the availability of the output is two cycles.

The processing continues cycle after cycle, producing a new output every clock cycle.

Using the pipeline diagram we can track how a particular input progresses through the system or see what all the stages are doing in any particular cycle.

## Pipeline Conventions

### Pipeline Conventions

**DEFINITION:**

A well-formed *K-Stage Pipeline* ("K-pipeline") is an acyclic circuit having exactly K registers on *every* path from an input to an output.

a COMBINATIONAL CIRCUIT is thus an 0-stage pipeline.

**COMPOSITION CONVENTION:**

Every pipeline stage, hence every K-Stage pipeline, has a register on its *OUTPUT* (not on its input).

**ALWAYS:**

The CLOCK common to all registers must have a period sufficient to cover propagation over combinational paths PLUS (input) register  $t_{PD}$  PLUS (output) register  $t_{SETUP}$ .

The LATENCY of a K-pipeline is K times the period of the system's clock.

The THROUGHPUT of a K-pipeline is the frequency of the clock.

**Figure 9.**

We'll define a K-stage pipeline (or K-pipeline for short) as an acyclic circuit having exactly K registers on every path from input to output. An unpipelined combinational circuit is thus a 0-stage pipeline.

To make it easy to build larger pipelined systems out of pipelined components, we'll adopt the convention that every pipeline stage, and hence every K-stage pipeline, has a register on its OUTPUT.

We'll use the techniques we learned for analyzing the timing of sequential circuits to ensure the clock signal common to all the pipeline registers has a period sufficient to ensure correct operation of each stage. So for every register-to-register and input-to-register path, we need to compute the sum of the propagation delay of the input register, plus the propagation delay of the combinational logic, plus the setup time of the output register. Then we'll choose the system's clock period to be greater than or equal to the largest such sum.


With the correct clock period and exactly K registers along each path from system input to system output, we are guaranteed that the K-pipeline will compute the same outputs as the original unpipelined combinational circuit.

The latency of a K-pipeline is K times the period of the system's clock. And the throughput of a K-pipeline is the frequency of the system's clock, i.e., 1 over the clock period.

## Ill-Formed Pipelines

### Ill-formed Pipelines

Consider a BAD job of pipelining:

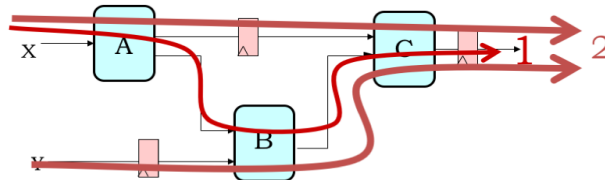

For what value of K is the following circuit a K-Pipeline?

ANS: none

Problem:

*Successive inputs get mixed: e.g.,  $B(A(X_{i+1}), Y_i)$ . This happened because some paths from inputs to outputs have 2 registers, and some have only 1!*

*This CAN'T HAPPEN on a well-formed K pipeline!*

**Figure 10.**


Here's a failed attempt at pipelining a circuit. For what value of K is the circuit a K-pipeline? Well, let's count the number of registers along each path from system inputs to system outputs.

The top path through the A and C components has 2 registers. As does the bottom path through the B and C components. But the middle path through all three components has only 1 register. Oops, this not a well-formed K-pipeline.

Why do we care? We care because this pipelined circuit does not compute the same answer as the original unpipelined circuit. The problem is that successive generations of inputs get mixed together during processing. For example, during cycle  $i + 1$ , the B module is computing with the current value of the X input but the previous value of the Y input.

This can't happen with a well-formed K-pipeline. So we need to develop a technique for pipelining a circuit that guarantees the result will be well-formed.

## A Pipelining Methodology

 

**Figure 11.**

Here's our strategy that will ensure if we add a pipeline register along one path from system inputs to system outputs, we will add pipeline registers along every path.

Step 1 is to draw a contour line that crosses every output in the circuit and mark its endpoints as the terminal points for all the other contours we'll add.

During Step 2 continue to draw contour lines between the two terminal points across the signal connections between modules. Make sure that every signal connection crosses the new contour line in the same direction. This means that system inputs will be one side of the contour and system outputs will be on the other side. These contours demarcate pipeline stages.

Place a pipeline register wherever a signal connection intersects the pipelining contours. Here we've marked the location of pipeline registers with large black dots.

By drawing the contours from terminal point to terminal point we guarantee that we cross every input-output path, thus ensuring our pipeline will be well-formed.


Now we can compute the system's clock period by looking for the pipeline stage with the longest register-to-register or input-to-register propagation delay. With these contours and assuming ideal zero-delay pipeline registers, the system clock must have a period of 8 ns to accommodate the operation of the C module. This gives a system throughput of 1 output every 8 ns. Since we drew 3 contours, this is a 3-pipeline and the system latency is 3 times 8 ns or 24 ns total.

Our usual goal in pipelining a circuit is to achieve maximum throughput using the fewest possible registers. So our strategy is to find the slowest system component (in our example, the C component)

and place pipeline registers on its inputs and outputs. So we drew contours that pass on either side of the C module. This sets the clock period at 8 ns, so we position the contours so that the longest path between any two pipeline registers is at most 8.

There are often several choices for how to draw a contour while maintaining the same throughput and latency. For example, we could have included the E module in the same pipeline stage as the F module.

## Pipeline Example

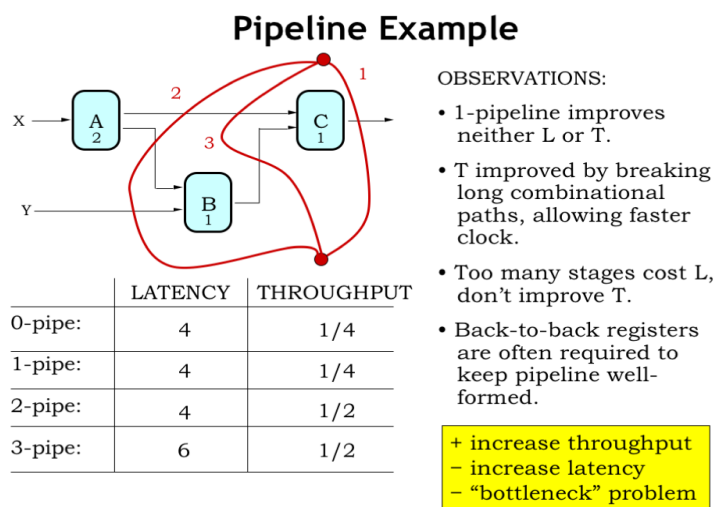

**Figure 12.**

Okay, let's review our pipelining strategy.

First we draw a contour across all the outputs. This creates a 1-pipeline, which, as you can see, will always have the same throughput and latency as the original combinational circuit.

Then we draw our next contour, trying to isolate the slowest component in the system. This creates a 2-pipeline with a clock period of 2 and hence a throughput of 1/2, or double that of the 1-pipeline.


We can add additional contours, but note that the 2-pipeline had the smallest possible clock period, so after that additional contours add stages and hence increase the system's latency without increasing its throughput. Not illegal, just not a worthwhile investment in hardware.

Note that the signal connection between the A and C module now has two back-to-back pipelining registers. Nothing wrong with that; it often happens when we pipeline a circuit where the input-output paths are of different lengths.

So our pipelining strategy will be to pipeline implementations with increased throughput, usually at the cost of increased latency. Sometimes we get lucky and the delays of each pipeline stage are perfectly balanced, in which case the latency will not increase. Note that a pipelined circuit will NEVER have a smaller latency than the unpipelined circuit.

Notice that once we've isolated the slowest component, we can't increase the throughput any further. How do we continue to improve the performance of circuits in light of these performance bottlenecks?

## Pipelined Components

 

**Figure 13.**


One solution is to use pipelined components if they're available! Suppose we're able to replace the original A component with a 2-stage pipelined version A-prime.

We can redraw our pipelining contours, making sure we account for the internal pipeline registers in the A-prime component. This means that 2 of our contours have to pass through the A-prime component, guaranteeing that we'll add pipeline registers elsewhere in the system that will account for the two-cycle delay introduced by A-prime.

Now the maximum propagation delay in any stage is 1 ns, doubling the throughput from 1/2 to 1/1. This is a 4-pipeline so the latency will be 4 ns.

This is great! But what can we do if our bottleneck component doesn't have a pipelined substitute? We'll tackle that question in the next section.

## How Do 6.004 Students Do Laundry?

 

**Figure 14.**

6.004 students work around the dryer bottleneck by finding a laundromat that has two dryers for every washer. Looking at the timeline you can see the plan, which is divided into 30-minute steps. The washer is in use every step, producing a newly-washed load every 30 minutes. Dryer usage is interleaved, where Dryer #1 is used to dry the odd-numbered loads and Dryer #2 is used to dry the even-numbered loads. Once started, a dryer runs for a duration of two steps, a total of 60 minutes. Since the dryers run on a staggered schedule, the system as a whole produces a load of clean, dry laundry every 30 minutes.

The steady-state throughput is 1 load of laundry every 30 minutes and the latency for a particular load of laundry is 90 minutes.

And now here's the take-home message from this example. Consider the operation of the two-dryer system. Even though the component dryers themselves aren't pipelined, the two-dryer interleaving system is acting like a 2-stage pipeline with a clock period of 30 minutes and a latency of 60 minutes. In other words, by interleaving the operation of 2 unpipelined components we can achieve the effect of a 2-stage pipeline.

## Back to Our Bottleneck...


### Back To Our Bottleneck...

Recall our earlier example...

- C – the slowest component – limits clock period to 8 ns.
- HENCE throughput limited to  $1/8\text{ns}$ .

We could improve throughput by

- Finding a pipelined version of C;
- OR ...
- *interleaving* multiple copies of C!

 


**Figure 15.**

Returning to the example of the previous section, we couldn't improve the throughput of our pipelined system past  $1/8\text{ ns}$  since the minimum clock period was set the by the 8 ns latency of the C module.

To improve the throughput further we either need to find a pipelined version of the C component or use an interleaving strategy to achieve the effect of a 2-stage pipeline using two instances of the unpipelined C component. Let's try that...

## Circuit Interleaving I

 

**Figure 16.**


Here's a circuit for a general-purpose two-way interleaver, using, in this case, two copies of the un-pipelined  $C$  component,  $C_0$  and  $C_1$ .

The input for each  $C$  component comes from a D-latch, which has the job of capturing and holding the input value. There's also a multiplexer to select which  $C$ -component output will be captured by the output register.

In the lower left-hand corner of the circuit is a very simple 2-state FSM with one state bit. The next-state logic is a single inverter, which causes the state to alternate between 0 and 1 on successive clock cycles. This timing diagram shows how the state bit changes right after each rising clock edge.

To help us understand the circuit, we'll look at some signal waveforms to illustrate its operation.

## Circuit Interleaving II

 

**Figure 17.**

To start, here are the waveforms for the CLK signal and our FSM state bit from the previous slide.

A new X input arrives from the previous stage just after the rising edge of the clock.

Next, let's follow the operation of the  $C_0$  component. Its input latch is open when FSM Q is low, so the newly arriving  $X_1$  input passes through the latch and  $C_0$  can begin its computation, producing its result at the end of clock cycle #2. Note that the  $C_0$  input latch closes at the beginning of the second clock cycle, holding the  $X_1$  input value stable even though the X input is starting to change. The effect is that  $C_0$  has a valid and stable input for the better part of 2 clock cycles giving it enough time to compute its result.

The  $C_1$  waveforms are similar, just shifted by one clock cycle.  $C_1$ 's input latch is open when FSM Q is high, so the newly arriving  $X_2$  input passes through the latch and  $C_1$  can begin its computation, producing its result at the end of clock cycle #3.

Now let's check the output of the multiplexer. When FSM Q is high, it selects the value from  $C_0$  and when FSM Q is low, it selects the value from  $C_1$ . We can see that happening in the waveform shown.


Finally, at the rising edge of the clock, the output register captures the value on its input and holds it stable for the remainder of the clock cycle.

The behavior of the interleaving circuit is like a 2-stage pipeline: the input value arriving in cycle  $i$  is processed over two clock cycles and the result output becomes available on cycle  $i + 2$ .

What about the clock period for the interleaving system? Well, there is some time lost to the propagation delays of the upstream pipeline register that supplies the X input, the internal latches and multiplexer,

and the setup time of the output register. So the clock cycle has to be just a little bit longer than half the propagation delay of the C module.

### Circuit Interleaving III

 

**Figure 18.**

We can treat the interleaving circuit as a 2-stage pipeline, consuming an input value every clock cycle and producing a result two cycles later.

When incorporating an N-way interleaved component in our pipeline diagrams, we treat it just like a N-stage pipeline. So N of our pipelining contours have to pass through the component.


## Combine Techniques

### Combine Techniques

We can combine interleaving and pipelining. Here,  $C'$  interleaves two  $C$  elements and has an effective  $t_{CLK}$  of 4 ns and a latency of 8 ns.

Since  $C'$  behaves as a 2-stage pipeline, two of our pipelining contours must pass through the  $C'$  component.

By combining interleaving with pipelining we move the bottleneck from the  $C$  element to the  $F$  element.

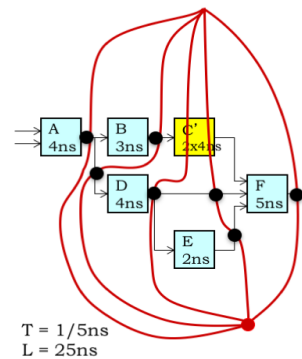

**Figure 19.**


Here we've replaced the slow unpipelined  $C$  component with a 2-way interleaved  $C$ -prime component.

We can follow our process for drawing pipelining contours. First we draw a contour across all the outputs. Then we add contours, ensuring that two of them pass through the  $C$ -prime component. Then we add pipeline registers at the intersections of the contours with the signal connections. We see that the contours passing through  $C$ -prime have caused extra pipeline registers to be added on the other inputs to the  $F$  module, accommodating the 2-cycle delay through  $C$ -prime.

Somewhat optimistically we've specified the  $C$ -prime minimum  $t_{CLK}$  to be 4 ns, so that means that the slow component which determines the system's clock period is now the  $F$  module, with a propagation delay of 5 ns.

So the throughput of our new pipelined circuit is 1 output every 5 ns, and with 5 contours, it's a 5-pipeline so the latency is 5 times the clock period or 25 ns.

## And Add a Little Parallelism...

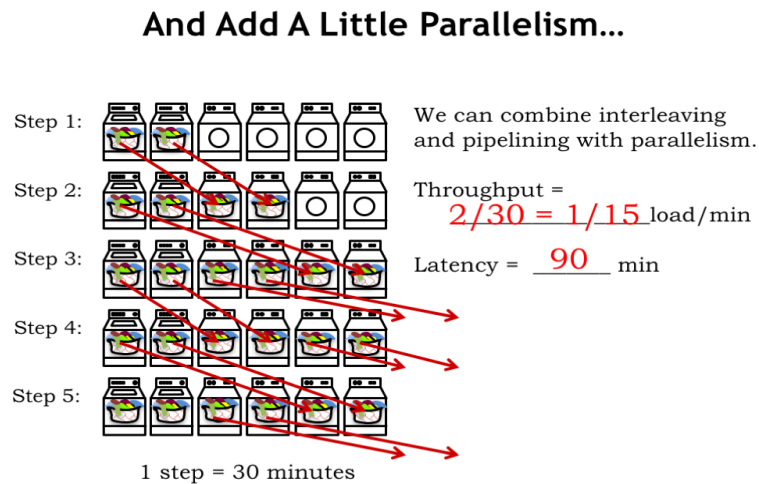


**Figure 20.**

By running pipelined systems in parallel we can continue to increase the throughput. Here we show a laundry with 2 washers and 4 dryers, essentially just two copies of the 1-washer, 2-dryer system shown earlier. The operation is as described before, except that at each step the system produces and consumes two loads of laundry.

So the throughput is 2 loads every 30 minutes for an effective rate of 1 load every 15 minutes. The latency for a load hasn't changed; it's still 90 minutes per load.

We've seen that even with slow components we can use interleaving and parallelism to continue to increase throughput. Is there an upper bound on the throughput we can achieve? Yes! The timing overhead of the pipeline registers and interleaving components will set a lower bound on the achievable clock period, thus setting an upper bound on the achievable throughput. Sorry, no infinite speed-up is possible in the real world.

## Control Structure Alternatives

 **Figure 21.**


We've been designing our processing pipelines to have all the stages operate in lock step, choosing the clock period to accommodate the worst-case processing time over all the stages. This is what we'd call a synchronous, globally timed system.

But what if there are data dependencies in the processing time, i.e., if for some data inputs a particular processing stage might be able to produce its output in a shorter time? Can we design a system that could take advantage of that opportunity to increase throughput?

One alternative is to continue to use a single system clock, but for each stage to signal when it's ready for a new input and when it has a new output ready for the next stage. It's fun to design a simple 2-signal handshake protocol to reliably transfer data from one stage to the next. The upstream stage produces a signal called *HERE-IS-X* to indicate that it has new data for the downstream stage. And the downstream stage produces a signal called *GOT-X* to indicate when it is willing to consume data. It's a synchronous system so the signal values are only examined on the rising edge of the clock.

The handshake protocol works as follows: the upstream stage asserts *HERE-IS-X* if it will have a new output value available at the next rising edge of the clock. The downstream stage asserts *GOT-X* if it will grab the next output at the rising edge of the clock. Both stages look at the signals on the rising edge of the clock to decide what to do next. If both stages see that *HERE-IS-X* and *GOT-X* are asserted at the same clock edge, the handshake is complete and the data transfer happens at that clock edge. Either stage can delay a transfer if they are still working on producing the next output or consuming the previous input.

## Self-Timed Example

 

**Figure 22.**

It's possible, although considerably more difficult, to build a clock-free asynchronous self-timed system that uses a similar handshake protocol. The handshake involves four phases. In phase 1, when the upstream stage has a new output and GOT-X is deasserted, it asserts its HERE-IS-X signal and then waits to see the downstream stage's reply on the GOT-X signal. In phase 2, the downstream stage, seeing that HERE-IS-X is asserted, asserts GOT-X when it has consumed the available input. In phase 3, the downstream stage waits to see the HERE-IS-X go low, indicating that the upstream stage has successfully received the GOT-X signal. In phase 4, once HERE-IS-X is deasserted, the downstream stage deasserts GOT-X and the transfer handshake is ready to begin again. Note that the upstream stage waits until it sees the GOT-X deasserted before starting the next handshake.


The timing of the system is based on the transitions of the handshake signals, which can happen at any time the conditions required by the protocol are satisfied. No need for a global clock here!

It's fun to think about how this self-timed protocol might work when there are multiple downstream modules, each with their own internal timing.

In this example, A's output is consumed by both the B and C stages. We need a special circuit, shown as a yellow box in the diagram, to combine the GOT-X signals from the B and C stages and produce a summary signal for the A stage.

Let's take a quick look at the timing diagram shown here. After A has asserted HERE-IS-X, the circuit in the yellow box waits until both the B and the C stage have asserted their GOT-X signals before asserting GOT-X to the A stage. At this point the A stage deasserts HERE-IS-X, then the yellow box waits until both the B and C stages have deasserted their GOT-X signals, before deasserting GOT-X to the A stage.

## Self-Timed Example (continued)

 

Elegant, timing-independent design:

- Each component specifies its own time constraints
- Local adaptation to special cases (eg, multiplication by 0)
- Module performance improvements automatically exploited
- Can be made asynchronous (no clock at all!) or synchronous

**Figure 23.**

Let's watch the system in action! When a signal is asserted we'll show it in red, otherwise it's shown in black.

A new value for the A stage arrives on A's data input and the module supplying the value then asserts its HERE-IS-X signal to let A know it has a new input.

At some point later, A signals GOT-X back upstream to indicate that it has consumed the value, then the upstream stage deasserts HERE-IS-X, followed by A deasserting its GOT-X output. This completes the transfer of the data to the A stage.

When A is ready to send a new output to the B and C stages, it checks that its GOT-X input is deasserted (which it is), so it asserts the new output value and signals HERE-IS-X to the yellow box which forwards the signal to the downstream stages.

B is ready to consume the new input and so asserts its GOT-X output. Note that C is still waiting for its second input and has yet to assert its GOT-X output.

After B finishes its computation, it supplies a new value to C and asserts its HERE-IS-X output to let C know its second input is ready.


Now C is happy and signals both upstream stages that it has consumed its two inputs. Now that both GOT-X inputs are asserted, the yellow box asserts A's GOT-X input to let it know that the data has been transferred. Meanwhile B completes its part of the handshake, and C completes its transaction with B and A deasserts HERE-IS-X to indicate that it has seen its GOT-X input. When the B and C stages see their HERE-IS-X inputs go low, they finish their handshakes by deasserting their GOT-X outputs,

and when they're both low, the yellow box lets A know the handshake is complete by deserting A's GOT-X input.

Whew! The system has returned to the initial state where A is now ready to accept some future input value.

This an elegant design based entirely on transition signaling. Each module is in complete control of when it consumes inputs and produces outputs, and so the system can process data at the fastest possible speed, rather than waiting for the worst-case processing delay.

## Control Structure Taxonomy

 

**Figure 24.**

Let's summarize what we've learned about controlling pipelined systems. The most straightforward approach is to use a pipeline with the system clock chosen to accommodate the worst-case processing time. These systems are easy to design but can't produce higher throughputs if the processing stages might run more quickly for some data values.

We saw that we could use a simple handshake protocol to move data through the system. All communication still happens on the rising edge of the system clock, but the specific clock edge used to transfer data is determined by the stages themselves.

It's tempting to wonder if we might adjust the global clock period to take advantage of data-dependent processing speedups. But the necessary timing generators can be very complicated in large systems. It's usually much easier to use local communication between modules to determine system timing than trying to figure out all the constraints at the system level. So this approach isn't usually a good one.

But what about locally-timed asynchronous systems like the example we just saw? Each generation of engineers has heard the siren call of asynchronous logic. Sadly, it usually proves too hard to produce a provably reliable design for a large system, say, a modern computer. But there are special cases, such as the logic for integer division, where the data-dependent speed-ups make the extra work worthwhile.

## Summary

### Summary

Latency (L) = time it takes for given input to arrive at output

Throughput (T) = rate at which new outputs appear

For combinational circuits:  $L = t_{PD}$  of circuit,  $T = 1/L$

For K-pipelines ( $K > 0$ ):

- always have register on output(s)
- K registers on every path from input to output
- Inputs available shortly after clock i, outputs available shortly after clock (i+K)
- $t_{CLK} = t_{PD,REG} + t_{PD}$  of slowest pipeline stage +  $t_{SETUP}$
- $T = 1/t_{CLK}$ 
  - more throughput  $\Rightarrow$  split slowest pipeline stage(s)
  - use replication/interleaving if no further splits possible
- $L = K \cdot t_{CLK} = K / T$ 
  - pipelined latency  $\geq$  combinational latency

### Figure 25.

We characterized the performance of our systems by measuring their latency and throughput. For combinational circuits, the latency is simply the propagation delay of the circuit and its throughput is just  $1/\text{latency}$ .

We introduced a systematic strategy for designing K-pipelines, where there's a register on the outputs of each stage, and there are exactly K registers on every path from input to output. The period of the system clock  $t_{CLK}$  is determined by the propagation delay of the slowest pipeline stage. The throughput of a pipelined system is  $1/t_{CLK}$  and its latency is  $K \cdot t_{CLK}$ .

Pipelining is the key to increasing the throughput of most high-performance digital systems.